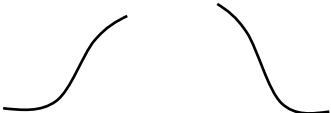
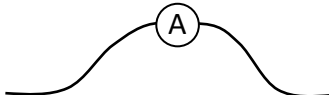




*To measure current
in this wire:*



*Break the circuit
somehow...*



*...and reconnect
through the ammeter.*