
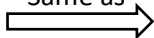


Same as 

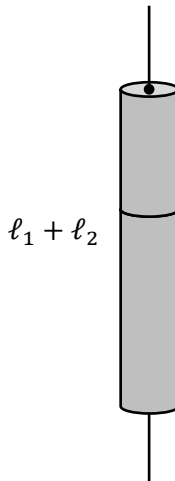

Write the equivalent resistance R_{eq} in terms of ℓ_1 , ℓ_2 , ρ , and A :

$$R_{eq} =$$

Use the result above to write R_{eq} in terms of R_1 , and R_2 .

$$R_{eq} =$$