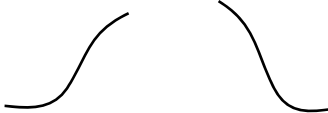
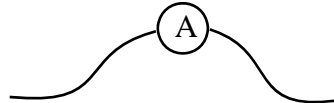




*To measure current  
in this wire:*



*Break the circuit  
somehow...*



*...and reconnect  
through the ammeter.*