
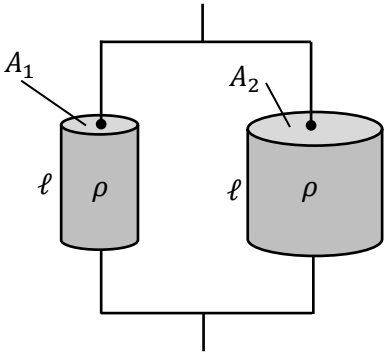


Same as

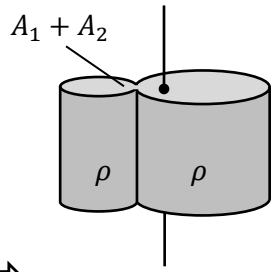

Write the equivalent resistance R_{eq} in terms of ρ, ℓ, and total area $(A_1 + A_2)$:

$R_{\text{eq}} =$

$R_1 =$ $R_2 =$

Use the result above to write R_{eq} in terms of R_1, and R_2. (Hint: start by writing $1/R_{\text{eq}}$.)